

Nickel Plate Installs 169 Miles of Color-light Automatics

*A-C. floating system with primary cells for track at cut-sections
—Unique polarized A. P. B. control*

By J. H. Oppelt

Supervisor of Signals, New York, Chicago & St. Louis

THE New York, Chicago & St. Louis has completed the installation of automatic signals between Conneaut, Ohio, and Arcadia, a distance of 169 miles, of which 117 miles is double track and 52 miles is single track. A total of 272 Union Switch & Signal Company Style R-2 color-light signals are included in the installation.


At several points where semaphore signals had been previously installed and at one interlocking plant, the semaphores were replaced with color-lights. Color-light signals were in service at five plants and at three plants where the semaphores were comparatively new, they were continued in service. In addition to adapting the automatic circuits to nine interlocking plants, provision had to be made also at 56 high-ways for automatic protection, 47 flasher lights, 6 wig-wag and 3 bells being used.


A-c. Floating System for Power

Line wires are placed on the bottom arm of the existing Western Union line, the wire stringing work being done by Western Union forces. Power is trans-


mitted at 440-volt, 60-cycle, single-phase on two No. 6 w.p. copper wires, attached to porcelain insulators on the two field pins. Control circuits are No. 10 w.p. copper attached to Western Union standard glass insulators. All wires are terminated on Ohio Brass Company dead-end strain insulators. Power is purchased from commercial power companies, the average distance between supply points being about 12 miles. At each point of supply a recording voltmeter is installed which provides a continuous record of the voltage. The voltage is stepped down from 440 to 110 through a Type-M transformer located on the crossarm so that no voltage higher than 110 is taken into the instrument case. Fused porcelain plug cut-outs are installed on the crossarm at each transformer.

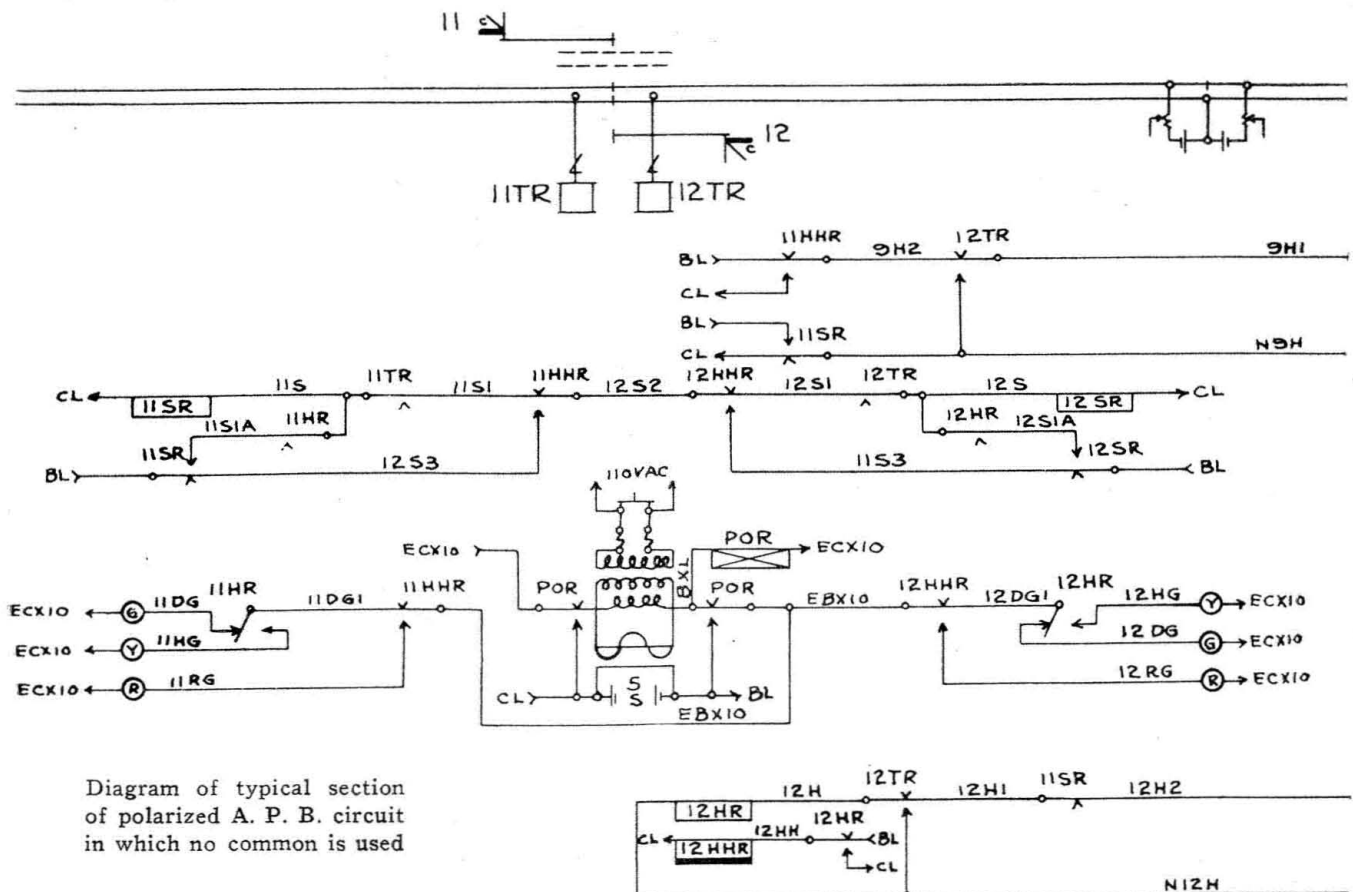The rails, which are all 90-lb. R. A. or 110-lb. R. E., are bonded partly with Armco wires and partly with Duplex Copperweld bonds. Continuous insulated joints are used throughout the installation. Kerite steel taped cable is used for all wire runs except shunt wires from rail to switch boxes where No. 9 Kerite



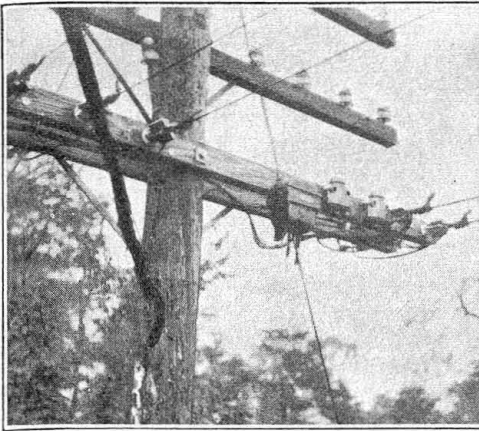

Transformer on crossarm

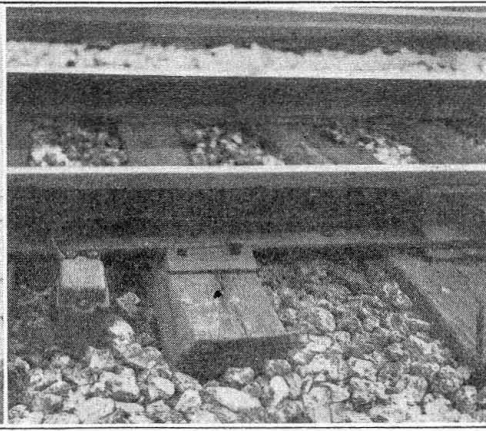

Raco parkway outlet




Flashlight crossing signal

A westbound train standing east of signal 1 will of course have signal 2 at "stop." This will mean that 2 HHR is de-energized and will send current in the reverse direction, through the coils of 4 HR. The reversal of 4 HR causes signal 4 to show a yellow or caution indication. As the train moves west past signal 1, it will drop 1 TR, thus opening the control of 1 HR. As 1 HR controls 1 HHR it also will drop, causing signal 1 to indicate "stop." 1 TR also opens 4 HR, then 4 HR opens 4 HHR, 4 HHR opens 6 HR, 6 HR opens 6 HHR; 6 HHR opens 8 HR, and 8 HR opens 8 HHR. Signals 4, 6 and 8 then show red or "stop" indications. 8 HHR dropping will reverse the current through 10 HR, causing it to reverse its polar contacts and signal 10 to show a yellow or "caution" indication. 10 HR in reversing will cause 12 HR to receive reversed current and signal 12 to show a yellow or "caution" indication. As signal 8 has a red marker which is always lighted, there are at this time two red lights which make 8 an absolute stop signal, holding all

eastbound trains from entering the block already occupied by the westbound train.

As the westbound train proceeds into circuit A1T it holds signal 1 at block by keeping 1 HR open and keeps all eastbound signals at block by keeping 4 HR open. As the train proceeds by signal 3 it will drop 3 TR, opening 3 HR, and as the train is still on circuit A1T, it will close the pick-up circuit for 3 SR before 3 HHR (which is slow-acting) opens. As 3 HHR opens, it will cause signal 3 to assume the "stop" position.

Relay 3 SR in picking up connects N1H to positive battery, and 3 HHR dropping connects 1H3 to negative battery. This completes the circuit for 1 HR as soon as the rear end of the train has proceeded far enough west so that it is clear of circuits 1T and 3T. Under the effect of this reversed power battery, 1 HR will pick up and reverse its polar points. 1 HR, in picking up, closes the circuit for 1 HHR. With 1 HR reversed and 1 HHR picked up, signal 1 will show a caution indication. Relay 3 SR opens the control of 4 HR

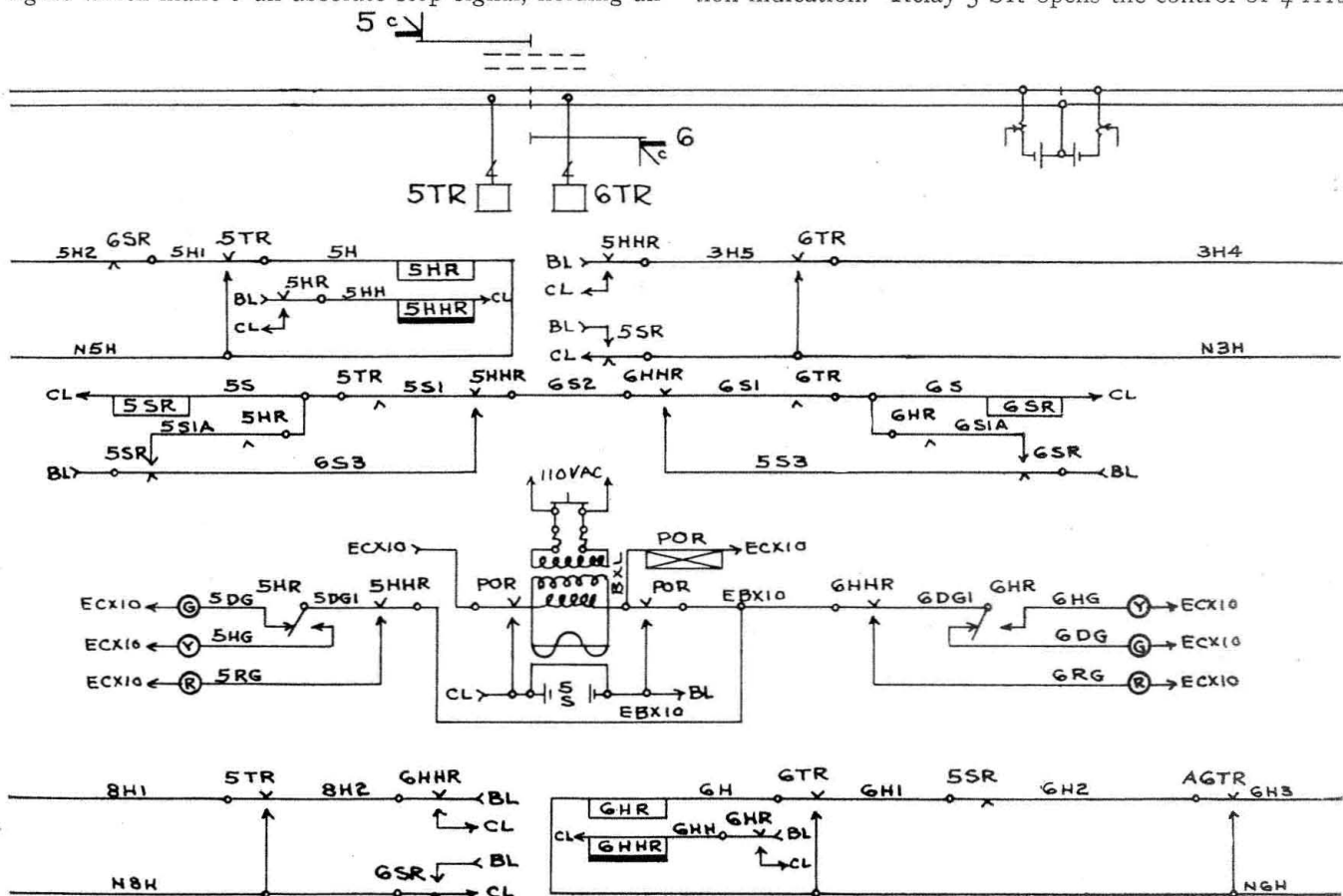


so that even though 3 TR picks up and closes 3 TPR, signal 4 will not clear, as there would then be a possibility of opposing trains passing signal 1 and signal 4 at the same instant.

As the train proceeds through circuits A6T and 6T, it holds the control of 3 HR open and also helps to keep signal 6 at stop. Of course signal 6 would remain at stop anyway, because 6 HHR is still down on this west-

ing red when changing from yellow to green. 3 SR in dropping connects the battery to 4 HR in the normal direction. 4 HR will pick up 4 HHR, giving a green or "proceed" indication to signal 4. 4 HHR will connect 6H4 to BL, but as 5 SR is picked up it will be impossible for 6 HR to pick up.

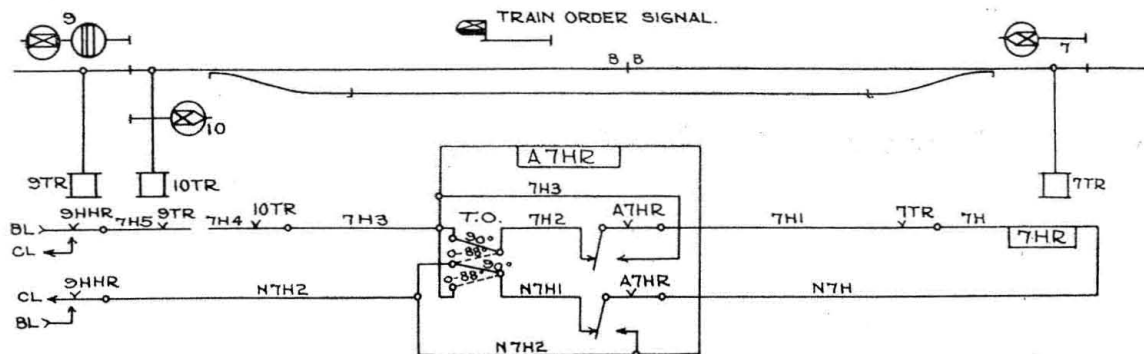As the train proceeds through 5T and 8T circuits, it will hold signal 5 at block by keeping 5 HR down and




Control of automatics extended through train-order signals without extra wires

bound move. As the train passes signal 5 it shunts 5 TR, opens 5 HR control and closes 5 SR before 5 HHR, which is slow-acting, gets a chance to open. As 5 HHR drops it places signal 5 to stop. 5 HHR connects 3H5 to CL and 5 SR connects N3H to BL as soon as the train clears 6 TR. 3 HR will receive reversed battery and will pick-up and reverse its polar contacts. This will allow signal 3 to display a caution indication when 3 HHR picks up.

3 HR in picking up releases 3 SR. With 3 SR down and 3 HHR up, 1 HR will receive battery through its coils in the normal direction which will energize the green light on signal 1, allowing it to indicate proceed. 1 HHR, being slow-acting, will not drop during the reversal of 1 HR and will prevent signal 1 from blink-

ing red when changing from yellow to green. 3 SR in dropping connects the battery to 4 HR in the normal direction. 4 HR will pick up 4 HHR, giving a green or "proceed" indication to signal 4. 4 HHR will connect 6H4 to BL, but as 5 SR is picked up it will be impossible for 6 HR to pick up.

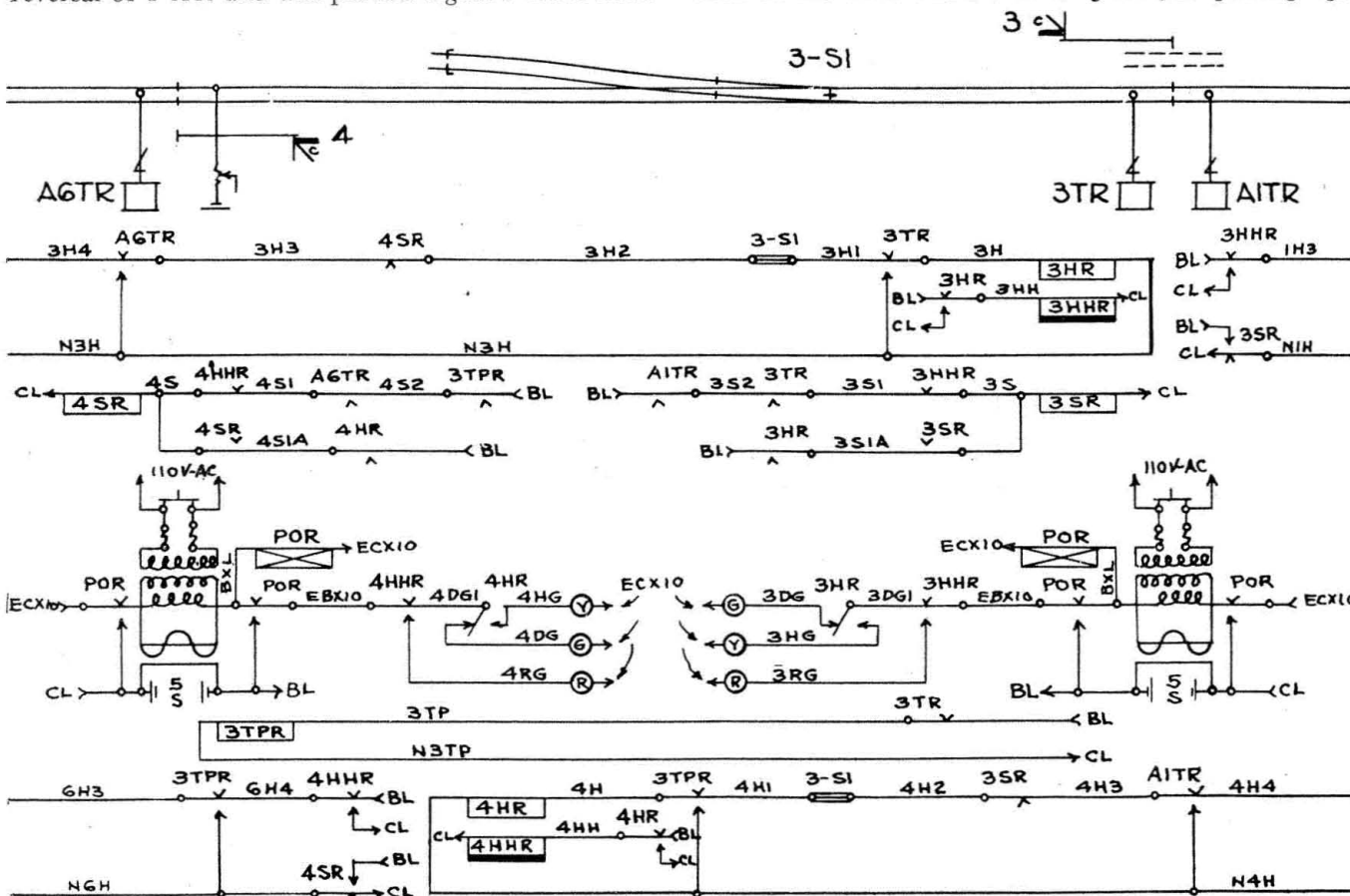As the train passes signal 7 shunts 7 TR, opening the control of 7 HR—7 HR opens 7 HHR—7 HHR in dropping, causes signal 7 to show stop—7 HHR connects 5 HR to negative battery and N5H to positive battery, thus allowing 5 HR to pick up as soon as the train clears 8 TR. 5 HR, in picking up,




picks up 5 HHR and also releases 5 SR. This puts normal battery on 3 HR, allowing its polar contacts to swing normal and light the green light on signal 3. 5 SR in dropping, puts normal battery on 6 HR, the latter picks up 6 HHR, which allows signal 6 to show green or proceed, 6 HHR picking up also puts normal battery on 8 HR, which picks up 8 HHR and clears signal 8. Relay 7 TR also keeps 10 HR open and signal 10 at block.

As the train proceeds to 10T circuit, 10 TR is shunted and keeps signals 7 and 10 at block. As the train passes signal 9 it shunts 9 TR, causing signal 9 and the opposing signals to the next passing track to show "stop," as described when the train passed signal 1. As 7 HR control is carried past absolute signal 9, so that two opposing trains cannot pass signals 7 and 10 at the same instant under caution indications, signal 7 will remain at block until the rear end of the westbound train has cleared 9T circuit.

In leaving 9T and entering 12T the train shunts 12 TR, keeping signal 9 and all opposing signals to the next siding at block. 9 TR, in picking up (with 9 HHR still down) puts reversed battery on 7 HR. 7 HR, in picking up reversed, picks up 7 HHR, causing signal 7 to show a yellow or caution indication. Relay 7 HR reversed and 7 HHR picked up, keep 5 HR reversed and hold signal 5 at caution.


As the train passes signal 11 it puts this signal red and picks up 11 SR. This causes signal 9 to show caution as soon as the rear end of the westbound train has cleared 12T. In clearing signal 9 to the caution indication, 9 HR picks up, in turn picking up 9 HHR and putting normal battery on 7 HR. This in turn causes signal 7 to show a green light and puts normal battery on 5 HR, causing signal 5 to show green.

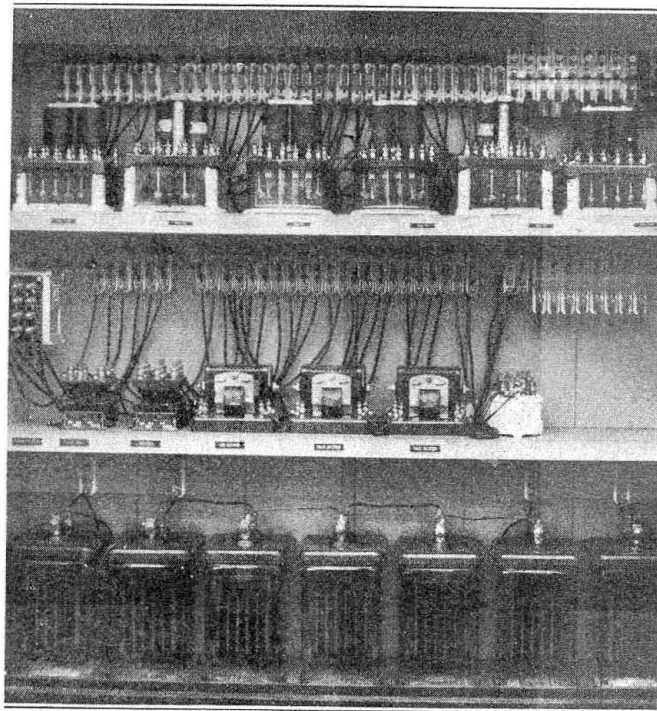
The control of the automatic signals is cut through



Interior of typical case

the mechanical train order signals and in order to accomplish this feature successfully a unique circuit was designed. The circuit at the train order signal is used to cause the automatic signals in the rear to show that some restricting signal is displayed ahead. The polarized relay is so controlled that, if either the train order signal is in a restricting position or signal 9 is at stop, signal 7 will indicate caution.

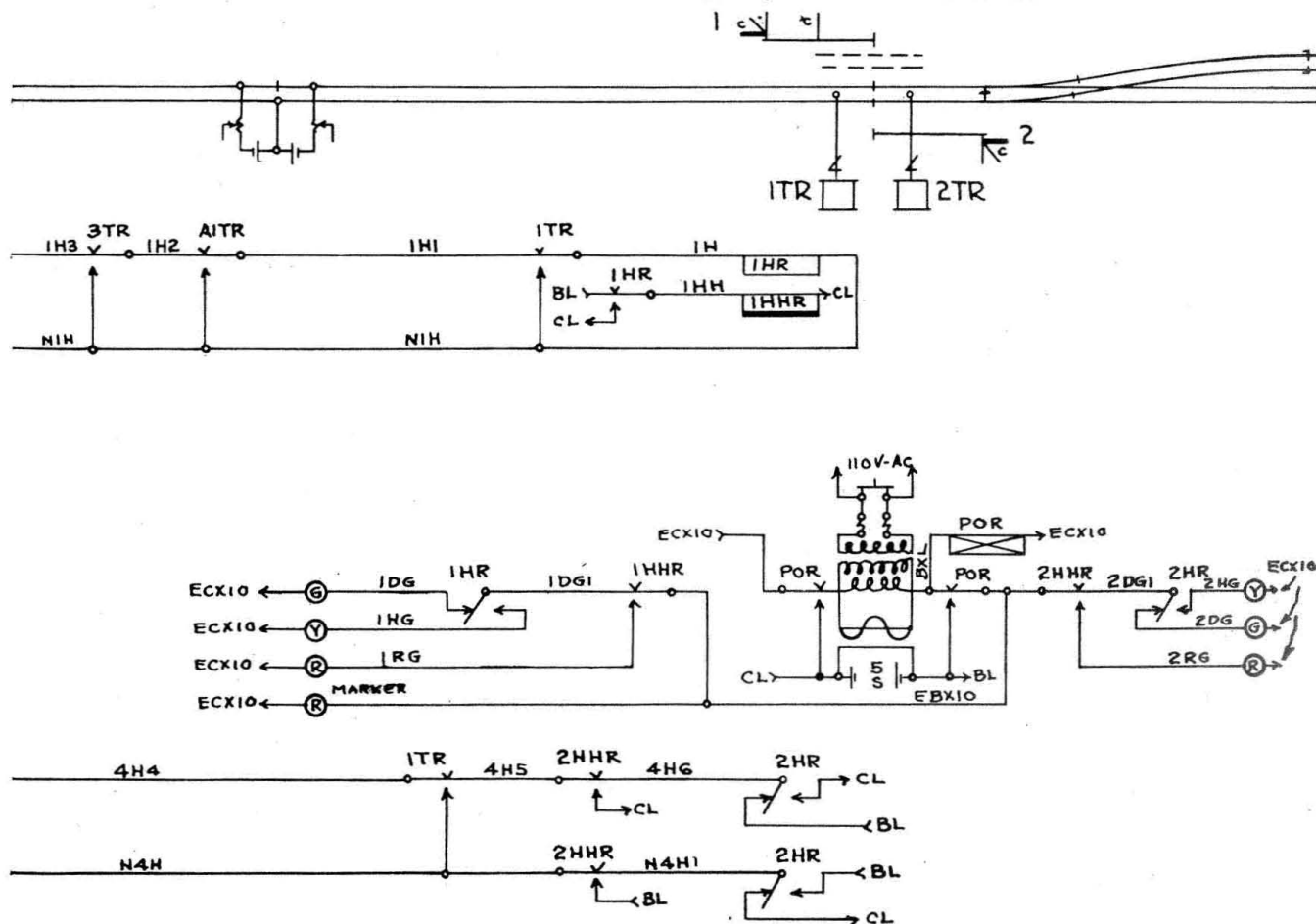

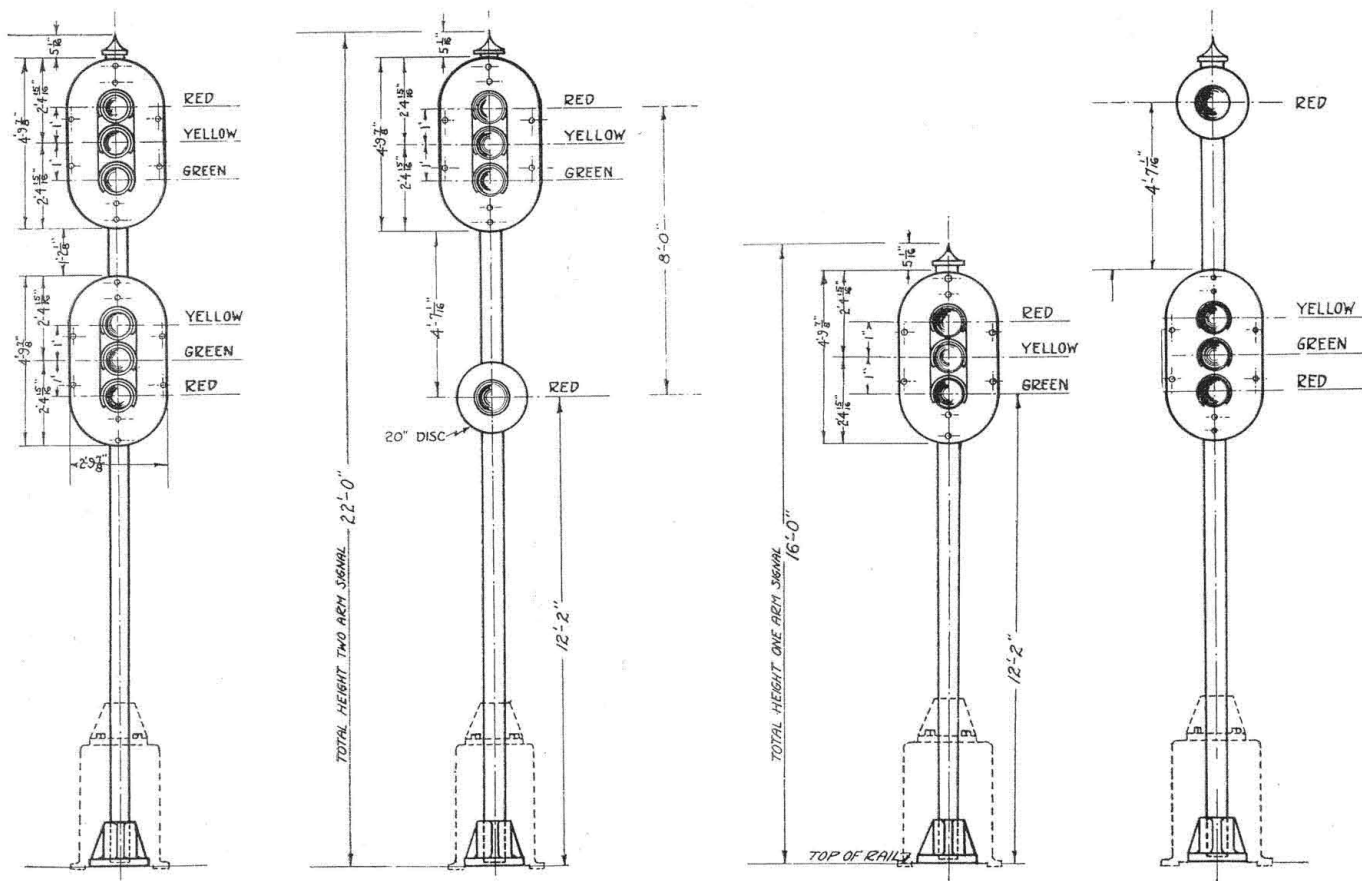

Diagrams showing arrangement of color-light units to secure maximum spacing between red lights

The additional polarized relay *A7 HR* is installed at the train order signal, which in the event that *9 HHR* changes the polarity of the circuit, relay *A7 HR* will reverse and eliminate the pole-changer at the train order signal from the circuit and allow the reversed current to pass through in such a way that *7 HR* will reverse. If *9 HR* remains in the normal position and the pole changing device at the train order signal is reversed, relay *A7 HR* will remain normal, but *7 HR* will re-

verse. In either case a train would receive a "caution" indication at signal 7.

The Union Switch & Signal Company furnished and installed all signal materials under the direction of J. T. Mallanny, field engineer. The railroad company furnished in place all foundations and all track insulation. H. M. Osinski, signal inspector, was in direct charge of all the signal construction work for the New York, Chicago & St. Louis.



Signal department officers of the Louisville & Nashville at a recent supervisors' conference